

## CDA 4253/EEL 4935 FPGA System Design

### Assignment #4

## 1 Description

Design a count-down timer with preset time with the following requirements.

1. Use the 7-segment display to show the remaining time `MM.SS` where `MM` are minutes and `SS` are seconds.
2. Use switches `sw15` - `sw8` to set time in minutes. The number set by these switches is a 2 digit BCD number.
3. Use switches `sw7` - `sw0` to set time in seconds. The number set by these switches is a 2 digit BCD number.
4. The range of minutes and seconds is from 0 to 59. If the inputs from switches are larger than 59, then those inputs should be treated as 59.
5. Use the button `BTNC` to reset the circuit.
6. Upon power-up/reset, the circuit reads the preset time from the switches and show it on the display. All LEDs light off.
7. When time is up where the display shows `00.00`, all LEDs should light on.
8. Make additional adjustment if necessary.

*Note: This design requires a clock divider that can produce ticks with a period of one second. To know how to implement such a clock divider, study the **Stopwatch** example in section 4.5.2 in Chu's book.*

*Design that does not work correctly on Basys3 FPGA boards will get no more than 70/100 points.*

## 2 Requirements

1. Create a folder `hw4-your-name` for this assignment, which holds design project files.
2. Create a `README` file to explain your work if necessary.
3. To submit, zip the entire folder `hw4-your-name`, and upload `hw4-your-name.zip` file to Canvas.

*Note: Make sure that your zipped file is in the ZIP format to avoid any potential issues in opening your files.*

*Note: Make sure that you copy all necessary files into the projects.*

4. *Make sure that you do NOT modify your work before the HW grading is finished in case that your original work needs to be examined.*